




Motilal Nehru National Institute of Technology Allahabad
Department of Electronics & Communication Engineering
End-Semester (Even) Examination (April-2017)
Programme: B. Tech, IV-Semester (ECE and EE)
Subject: Digital Electronics (EC-1402)

Time: 3:00 Hours

Maximum Marks: 60

NOTE: Attempt all the questions and assume the necessary data if required.

 - Q1** Design a clocked sequential circuit using T flip-flops for the following state diagram. Use the state reduction if possible. (8)



- Q2** (a) A combinational circuit is defined by the functions: (8)
 $F_1(A, B, C) = \sum m(3, 5, 6, 7)$ and $F_2(A, B, C) = \sum m(0, 2, 4, 7)$
 Implement the circuit using PLA.
- ★ (b) Design and implement a BCD to seven segment decoder circuit.
- Q3** (a) Design and implement a 4-bit random sequence generator using synchronous sequential circuit. (8)
 (b) What is race around condition in a J-K Flip-Flop? Explain how it occurs? Suggest the methods to overcome the race-around difficulty.
- Q4** (a) What are the different performance parameters of a logic family and explain them. (8)
 (b) Verify the truth table of NAND gate using TTL and CMOS logic family.
- Q5** (a) Design and explain the operation of Astable multivibrator. And derive the expression for duty cycle. (8)
 (b) With the help of an example explain the design methodologies of a digital VLSI chip and compare them

- Q6 (a) With the help of an example explain the operation of different shift registers. And state their applications. (8)
- (b) Design an asynchronous counter with counting sequence as 2, 3, 4, 5, 6, 2, 3 (8)
- Q7 (a) Realize S-R and D flip-flops using J-K flip-flop. (8)
- (b) Design and implement a 2-bit comparator circuit. And also explain its advantages. (4)
- Q8 Design a combinational circuit defined by the following three functions: (4)
- $$F_1 = x'y' + xyz'$$
- $$F_2 = x' + y$$
- $$F_3 = xy + x'y'$$
- Design a circuit with a decoder and external gates.

END