



Motilal Nehru National Institute of Technology Allahabad
Department of Electronics and Communication Engineering
End Semester (odd) Examination 2016

Session: 2016 - 17

B. Tech. III Semester (ECE)
Principles of Electronics Engineering (EC-1301)

Time: 03hrs

Max. Marks: 60


Instructions: Answer all the questions in sequence only and assume suitable data wherever necessary. All symbols and notations have their usual meaning.

1. (i) Implement the following functions using the don't-care conditions. Assume that both the normal and complement inputs are available.
- (a) $F = A'B'C' + AB'D + A'B'CD'$ with no more than two NOR gates.
 $d = ABC + AB'D'$
- (b) $F = B'D + B'C + ABCD$ with NAND gates.
 $d = A'BD + AB'C'D'$
- (ii) (a) Find 16's complement of $(AF3B)_H$. 50C5
(b) Convert AF3B to binary.
(c) Find 2's complement of the result in (b).
(d) Convert the result of (c) to hexadecimal and compare with answer in (a). [4]
- (iii) A Boolean function f of two variables x and y is defined as follows:
 $f(0, 0) = f(0, 1) = f(1, 1) = 1$; $f(1, 0) = 0$.
Assuming complements of x and y are not available, implement the function f using minimum number of gates (use only 2-input NOR gates and 2-input OR gates). [3]
2. (i) Discuss the temperature dependence of $V - I$ characteristics of a pn junction diode. [3]
- (ii) A 10 V zener diode is used to regulate the voltage across a variable load resistor. The input voltage varies between 13 V and 16 V, the load current varies between 10 mA and 85 mA. The minimum zener current is 15 mA. Calculate (a) Value of the series resistance (b) Power rating of the series resistance. 602 0.6 [4]
- (iii) Explain the working of a bridge rectifier with necessary circuit and waveforms. [4]

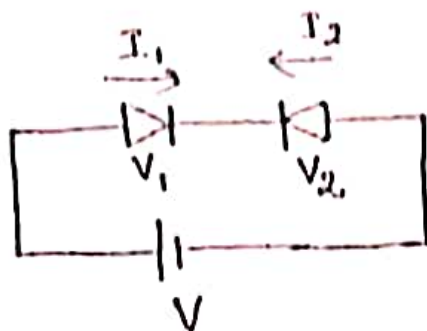(iv) Two identical diodes are connected in series as shown below. Show that

$$\exp\left(\frac{qV_1}{kT}\right) + \exp\left(\frac{qV_2}{kT}\right) = 2$$

Calculate the voltage drop across each diode, assuming that the current through the reverse biased diode is I_0 . [4]



3. (i) Draw a sketch to show the current components in a transistor and briefly explain the origin of each. Derive an expression of I_C in terms of I_B and I_{CBO} . Define α_{dc} and β_{dc} . [4]

(ii) Draw the input and output characteristics of a transistor connected in CE configuration. From these characteristics, how will you determine h -parameters? [3]

(iii) What is the need for biasing a transistor? What is meant by Q-point? Draw the collector-to-base bias circuit and derive an expression for the stability factor. [4]

(iv) If the various parameters of a CE amplifier which uses the self bias method are $V_{CC} = 12V$, $R_1 = 10k\Omega$, $R_2 = 5k\Omega$, $R_C = 1k\Omega$, $R_E = 2k\Omega$, and $\beta = 100$, find the coordinates of the operating point, assuming the transistor to be of silicon. [4]

4. (i) Explain the distinct regions of the output characteristics of a JFET. [4]

(ii) What is a MOSFET? How many types of MOSFETs are there? Briefly explain its working principle. [3]

(iii) What are the characteristics of an ideal Operational amplifier? Draw the schematic symbol of an Operational amplifier and list the different terminals with their functions. [4]

(iv) Discuss the applications of Operational amplifier as adder and subtractor. [4]