




Motilal Nehru National Institute of Technology Allahabad
Department of Electronics & Communication Engineering
End-Semester (odd) Examination (November-2016)
Programme: B. Tech (EE), III-Semester
Subject: Principles of Electronics (EC-1304)

Time: 3:00 Hours

Maximum Marks: 60

NOTE: Attempt all the questions and assume the necessary data if required.

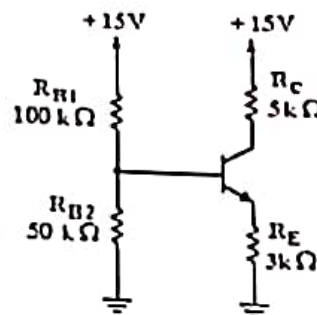- Q1 Draw and explain the (a) Logarithmic amplifier (for two input signals only) and (b) Integrator circuits using operational amplifier. (8)
- Q2 With the help of neat diagram explain the operation of n-channel MOSFET and its input and output characteristics. (7)
- Q3 Draw and explain the hybrid parameter model of a BJT transistor with suitable diagrams. Also, derive the expression for current gain, voltage gain, power gain and input impedance. (8)
- Q4 Analyze the given circuit to determine all node voltages (V_C , V_E) and branch currents (I_B , I_C , I_E). Assume $\beta = 100$. (7)



- Q5 Consider a pn junction in equilibrium at room temperature ($T=300$ K) for which the doping concentrations are $N_A=10^{18}/\text{cm}^3$ and $N_D=10^{16}/\text{cm}^3$ and the cross sectional area $A=10^{-4} \text{ cm}^2$. Calculate p_p , n_{p0} , n_n , p_{n0} , V_0 , W , x_n and x_p . Use $n_i=1.5 \times 10^{10}/\text{cm}^3$. (8)
- Q6 For a given function $F(a, b, c, d) = \sum m(0, 1, 2, 4, 6, 7, 8, 9, 10, 11, 12, 15)$ find the followings: (7)
- (a) Minimized expression
- (b) Implement the minimized function using two input NOR gates.
- Q7 Convert the following numbers from the given bases to the bases indicated: (8)
- (a) Decimal 225.225 to binary, octal and hexadecimal.
- (b) Binary 11010111.110 to decimal, octal and hexadecimal.
- (c) Octal 623.77 to decimal, binary and hexadecimal.
- (d) Hexadecimal 2AC5.D to decimal, octal and binary.
- Q8 Explain the operation and characteristics of Tunnel and Varactor diode. (7)