

Motilal Nehru National Institute of Technology Allahabad

Class: B. Tech. (EE), 4th Semester

Subject: Networks and Systems (EE-1301)

Session: Odd Semester (2015-16), Examination: End-Sem. Exam

Max. Time: 3 Hours

Max. Marks: 60 marks

Note: Attempt ALL questions. Marks are indicated next to them. Q7 is compulsory.

1. Attempt Any Two of the following:

- (a) Find the value of the current 'I' flowing through 50Ω Resistor in the bridge network shown in Figure 1(a). [05]
- (b) What is the power loss in the 10Ω resistor of the circuit in Figure 1(b)? [05]
- (c) If V_L represents the drop across R_L in Figure 1(c), find the current across R_L utilizing Thevenin's theorem. Assume $R_L = 10\Omega$ and a factor in the dependent current source as 0.5. [05]
- (d) Find Thevenin's equivalent circuit for the network shown in Figure 1(d) at the left of terminals x-y. [05]

2. (a) Derive the mathematical expression of cascade parameters in terms of h-parameters for a 2-port network. [05]

(b) In the circuit shown in Figure 2(b), find the h-parameter. [05]

(c) The Z-parameters of a two-port network are [05]

$$Z_{11}=10\Omega, Z_{22}=20\Omega, Z_{12}=Z_{21}=5\Omega.$$

(i) Find the ABCD parameters of this two-port network.

(ii) Find its equivalent T-network.

3. Attempt Any Three of the following:

(a) In a series RC circuit, the resistance is of 2Ω while the capacitor is of $\frac{1}{4} F$. Find the transfer function of voltage and the drop across the capacitor assuming the supply voltage to be $V_o(t)=t u(t)$. [05]

(b) A RL series circuit is energized by a voltage $V_o(t)=3t u(t)$. Find $i(t)$. Assume $R=2\Omega, L=1H$. [05]

(c) Find $V_C(t)$ and $I_L(t)$ in the circuit of Figure 3(c) assuming zero initial conditions. [05]

(d) A triangular pulse waveform is shown in Figure 3(d) by waveform analysis, draw the component functions. [05]

4. (a) Write pole zero concept in context of stability of a system. [02]

(b) Check whether following is Hurwitz or not! [06]

(i) $s^5 + s^3 + s$

(ii) $s^5 + 3s^4 + 3s^3 + 4s^2 + s + 1$

(c) Check whether following is PRF or not! [04]

$$Z(s) = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$$

(d) Realize following network in Cauer and Foster network forms: [08]

$$Z(s) = \frac{6s^3 + 5s^2 + 6s + 4}{2s^3 + 2s}$$

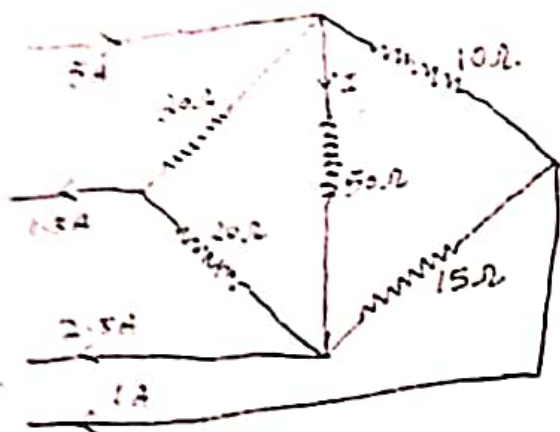


Figure 1(a)

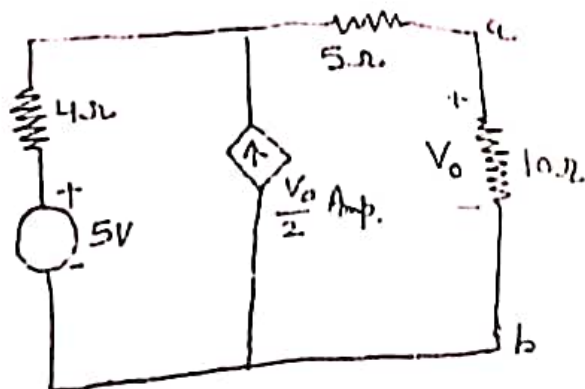


Figure 1(b)

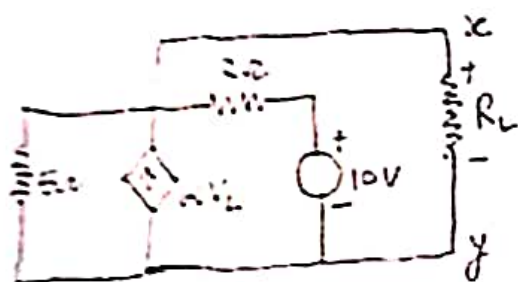


Figure 1(c)

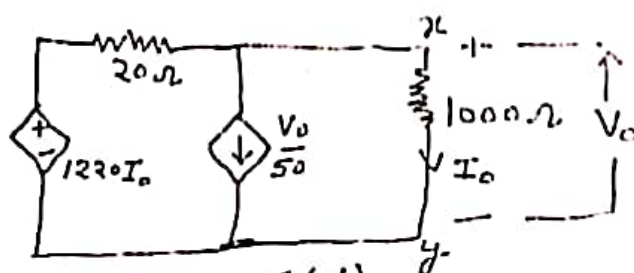


Figure 1(d)



Figure 2(b)

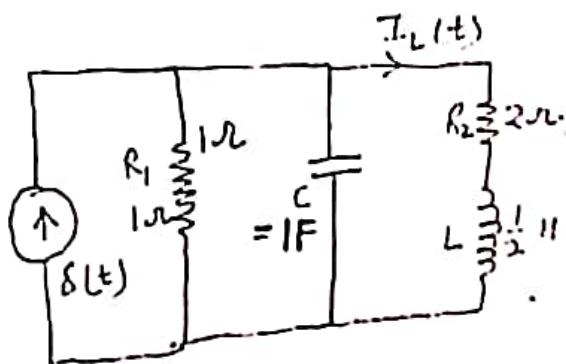


Figure 3(c)

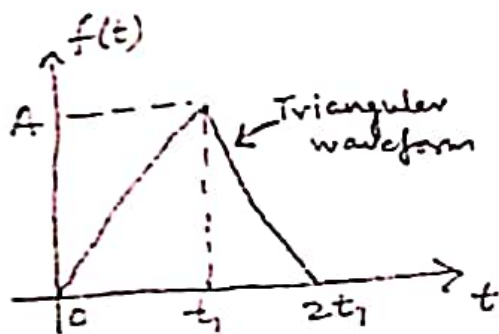


Figure 3(d)